
 Faculty of
 Engineering and Applied Science

Engineering 4862 Microprocessors

Lecture 23

 Cheng Li
 EN-4012
 l1cheng@engr.mun.ca

Input / Output Instructions

- Since 8086/88 has a 16-bit data bus internally, it is capable of transferring 16-bit data to or from AX. → **This requires having two port addresses, one for each byte!**
- Example: AX = 9876H, Port # = 40H
 OUT 40H, AX
 → Port 40 ← 76H (AL), Port 41 ← 98H(AH)
- For 8086, takes one bus cycle to complete the transfer, for 8088, two bus cycles are required

Engr 4862 Microprocessors

Example: 8 LEDs

- We only want the latch to load values from the data bus when the microprocessor outputs to the correct port #
 - Suggestion 1: Decode the address directly
 - Suggestion 2: Use a decoder such as the 3x8 74LS138 with lines from the address bus

Engr 4862 Microprocessors

I/O Design


- When designing an I/O port, ensure that the port is only active when selected by the microprocessor
 - Use latches (output) and buffers (input) to isolate the I/O port circuitry from the address and data bus
 - Use the correct combinatorial logic circuitry and/or decoders with address bus to select the port

Engr 4862 Microprocessors

Output Design Example: 8 LEDs

- This is a byte-wide output port
- The LEDs cannot be connected directly to data bus
 - Difficult to select the LEDs
 - LEDs would only display value for very short period of time (about 400ns, or 2 clock cycles)
 - Only when data bus carries the correct signal
 - Microprocessor cannot sink enough current

Engr 4862 Microprocessors

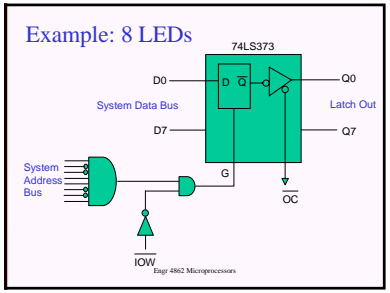



Input / Output Instructions

- For 8-bit port

IN AL, Port #		OUT Port #, AL
MOV DX, Port #	MOV DX, Port #	
IN AL, DX	OUT DX, AL	
- For 16-bit port

IN AX, Port #		OUT Port #, AX
MOV DX, Port #	MOV DX, Port #	
IN AX, DX	OUT DX, AX	

Engr 4862 Microprocessors

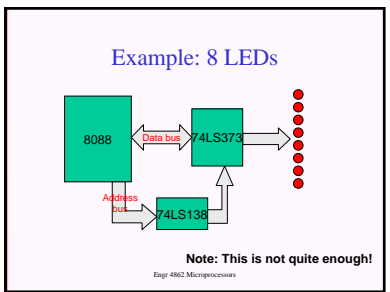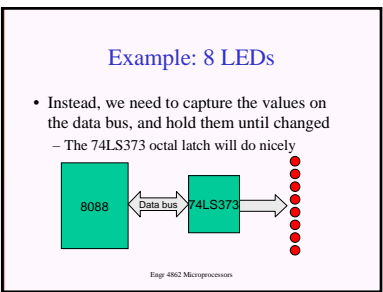



Example: 8 LEDs

The 74LS138 does not have enough power to drive an LED.

The device can sink enough current for the LED to light (15 to 20 mA).

Eogr 4862 Microprocessors

Example: 8 LEDs

- We only want the latch to load values from the data bus when the microprocessor outputs to the correct port #
 - Suggestion 1: Decode the address directly
 - Suggestion 2: Use a decoder such as the 3x8 74LS138 with lines from the address bus

Eogr 4862 Microprocessors

Example: 8 LEDs

- How do we connect the LEDs?
 - 2 possibilities

Eogr 4862 Microprocessors

Bus Cycles for outputting

- Assume the port address is 99H → OUT 99H, AL
 - T1: address 99H is provided to address bus A0 – A7 through AD0 – AD7 and ALE signal
 - T2: IOW is provided and the contents of AL are released into the data bus pins AD0 – AD7
 - T3: signal propagates to the destination port
 - T4: the content of AL are latched into the 74LS373 with the IOW going from low to high

Eogr 4862 Microprocessors

Example: 8 LEDs

Eogr 4862 Microprocessors

Example: 8 LEDs

Eogr 4862 Microprocessors

Example: 8 LEDs


- Instead, we need to capture the values on the data bus, and hold them until changed
 - The 74LS373 octal latch will do nicely

Eogr 4862 Microprocessors

Example: 8 LEDs

Note: This is not quite enough!

Eogr 4862 Microprocessors

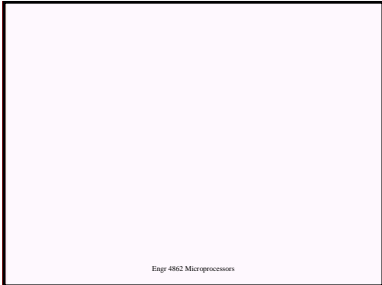

Example: 8 LEDs

The 74LS138 does not have enough power to drive an LED.

The device can sink enough current for the LED to light (15 to 20 mA).

180ohms

Engg 4862 Microprocessors

Example: 8 Switches

- Now we will look at an 8-bit input port.
- The procedure to select the port is similar to the output case
 - Use IORD* instead of IOWR*

Engg 4862 Microprocessors

Example: 8 LEDs

- How do we connect the LEDs?
 - 2 possibilities

Engg 4862 Microprocessors

Bus Cycles for outputting

- Assume the port address is 99H → OUT 99H, AL
 - T1: address 99H is provided to address bus A0 – A7 through AD0 – AD7 and ALE signal
 - T2: IOW is provided and the contents of AL are released into the data bus pins AD0 – AD7
 - T3: signal propagates to the destination port
 - T4: the content of AL are latched into the 74LS373 with the IOW going from low to high

Engg 4862 Microprocessors

Example: 8 Switches

- We cannot use a latch to separate the switches from the microprocessor
 - We only want the switch values to be on the data bus when the microprocessor asks for it
 - A latch would constantly drive the bus!

Engg 4862 Microprocessors

Example: 8 LEDs


Engg 4862 Microprocessors



Example: 8 Switches

- The device of interest here is the 74LS244 tristate buffer (unidirectional)
 - NOT the same as the 74LS245 transceiver (bidirectional)
- Tristate:
 - One of three states: on (1), off (0), or open (Z)
 - In the open state, the buffer does not drive the data bus

Engg 4862 Microprocessors

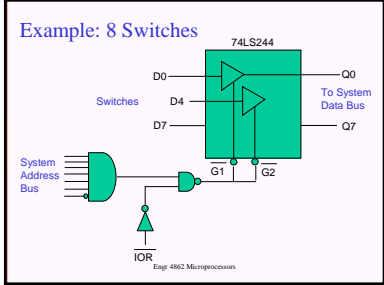


- ### Programmable I/O
- The previous examples are good for many applications, but sometimes a more powerful and flexible solution is needed.
 - The 8255 Programmable Peripheral Interface (PPI) is a 40-pin DIP IC that provides 3 programmable I/O ports, A, B, and C.
 - One can program the individual port to be input or output port, economical and flexible than 74LS373, 73LS244, which must be hard wired)

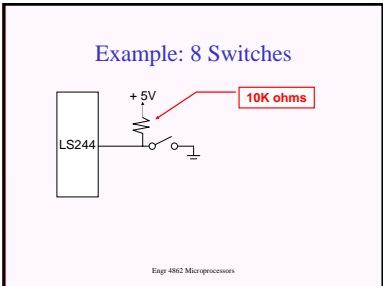- ### Example: 8 Switches
- How do we set up the switches?
 - When open, one logic level
 - When closed, the other logic level

- ### Summary
- Since the data provided by the CPU to the port is on the system data bus for a limited amount of time (50-1000ns), it must be latched before it is lost
 - In order to prevent any unwanted data from coming into the system data bus, all input devices must be isolated through the tri-state buffer
 - The 74LS244 not only plays this role, but also provides the incoming signals sufficient strength (boosting) to travel all the ways to the CPU.
 - As general, every device (memory, peripherals) connected to the global data bus must have a latch or tri-state buffer

- ### Programmable I/O
- How are is it programmable?
 - Configure each port as input or output
 - Different modes of operation
 - You must initialize the PPI via software commands
 - Send a control byte to the device's control register port



- ### Pin Description
- PA0 – PA7: Port A / All / input/output/bidirectional
 - PB0 – PB7: Port B / All / input/output
 - PC0 – PC7: Port C / All / input/output
 - Can be split into two parts: Upper (PC7 – PC4) and Lower (PC3 – PC0).
 - Each can be used for input or output.
 - Any of PC0 – PC7 can be programmed.
 - \overline{RD} and \overline{WR} : control signal input to 8255
 - \overline{IOR} and \overline{IOW} in peripheral I/O
 - \overline{MEMR} and \overline{MEMW} in memory-mapped I/O

Pin Description

- **RESET:** Active high input signal to 8255
 - Used to clear the internal control register
 - When activated, all ports are initialized as **input ports**.
 - Usually connect to the RESET output of the system bus or ground
- **A0, A1, and CS**
 - CS selects the entire chip, A0 and A1 select the specified port
 - Used to access port A, B, C,

CS	A1	A0	Select
0	0	0	Port A
0	0	1	Port B
0	1	0	Port C
0	1	1	Control Reg.
1	x	x	Not Selected


Engg 4862 Microprocessors

Mode Selection

- **Mode 0:** simple I/O
 - Any ports: A, B, CL, CU. No control of individual bits
- **Mode 1:** I/O (ports A and B) with handshaking (port C)
 - Synchronizes communication between an intelligent device (printer)
- **Mode 2:** Bi-directional I/O with handshaking
 - Port A: bidirectional I/O with handshaking through port C
 - Port B: Simple I/O or in handshake mode 1
- **BSR Mode:** Bit set/reset
 - Only the individual bits on Port C can be programmed

Engg 4862 Microprocessors

Control Word of 8255

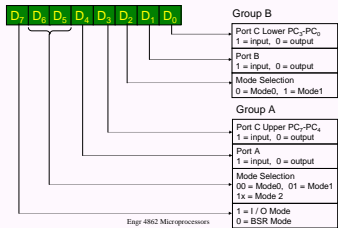

Engg 4862 Microprocessors

8255 Design Example

- **Mode 0**
 - Any of ports A, B, C can be programmed as input or output
 - Port can not be both an input and output port at the same time
 - Port C can be programmed with CL, CH separately
 - Example:


Engg 4862 Microprocessors

Mode Selection

- It's the control register that must be programmed to select the operation mode of the three ports: A, B, and C
- The 8255 chip is programmed in any of the above modes by sending a byte (control word) to the control register of the 8255

Engg 4862 Microprocessors

8255 Design Example

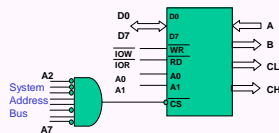

Engg 4862 Microprocessors